

CADD LAB EXPERIMENTS LIST


3rd Semester CADD Lab



PES UNIVERSITY
Electronic City Campus
Vinay Reddy

Write the SystemVerilog code for the following Combinational Circuits and implement them on the FPGA Board

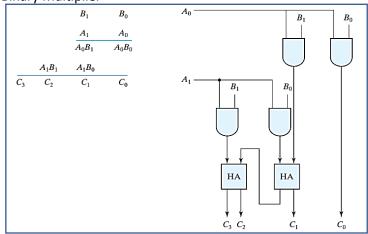- 1. Full Adder Dataflow Style
- 2. Full Adder Structural Style
- 3. Full Adder Using Two Half Adders (Structural Style)
- 4. Logic Gates (All Gates)
- 5. 4:1 Mux Dataflow Style
- 6. 4:1 Mux using 2:1 Mux (Structural Style)
- 7. 4:1 Mux Using two level logic (Structural Style)
- 8. 2 bits wide 4:1 Mux Dataflow Style
- 9. Binary to Gray code converter
- 10. Gary to Binary code converter
- 11. Binary to Excess 3 code converter
- 12. 4-bit Ripple Carry Adder
- 13. 4 to 2 Priority Encoder
- 14. 8 to 3 Priority Encoder with a valid bit
- 15. 3 to 8 Decoder
- 16. 2 to 4 Decoder
- 17. Write an HDL module for a hexadecimal seven-segment display decoder. The decoder should handle the digits A, B, C, D, E, and F as well as 0–9.
- 18. Full Adder using 4:1 Mux
- 19. 2-bit Magnitude Comparator
- 20. Half Subtractor
- 21. Full Subtractor
- 22. Tristate Buffer
- 23. Binary Multiplier



- 24. Full Adder with 3 to 8 Decoder
- 25. BCD Adder
- 26. Four-bit adder-subtractor (with overflow detection)
- 27. Four-bit adder with carry lookahead
- 28. 2:1 Mux using Conditional Operator
- 29. 1:8 Demultiplexer
- 30. 4-bit Parallel Subtractor

Write the SystemVerilog code for the following Sequential Circuits and implement them on the FPGA Board

- 31. D latch, SR Latch Dataflow Style, Structural Style
- 32. D FF, SR FF, JK FF, T FF Dataflow Style, Structural Style, Behavioural Style
- 33. Tristate Buffer
- 34. Tristate Inverter
- 35. FFs with Synchronous reset
- 36. FFs with Asynchronous reset
- 37. Enabled FFs and Latches
- 38. FSM Non-Overlapping Sequence Detectors Moore Model
- 39. FSM Non-Overlapping Sequence Detectors Mealy Model
- 40. FSM Overlapping Sequence Detectors Moore Model
- 41. FSM Overlapping Sequence Detectors Mealy Model
- 42. Synchronous Up Down Counter
- 43. Synchronous MOD Counter
- 44. Ring & Johnson Counter
- 45. Asynchronous Counter